

PRACTICAL-7

AIM: To Verify 1×4 Demultiplexer using Truth Table and Logic Diagram

- To verify 1×4 Demultiplexer using truth table and logic diagram :
- A 1×4 demultiplexer is a digital logic device that takes a single input and routes it to one of several outputs based on the value of the control signals. To verify the functionality of a 1×4 demultiplexer, you can use a truth table and a logic diagram.

i). Boolean Expression :-

$$\bar{S}_1 \bar{S}_0 A + \bar{S}_1 S_0 A + S_1 \bar{S}_0 A + S_1 S_0 A$$

ii). Truth Table :-

| INPUTS | | OUTPUTS | | | |
|--------|-------|---------|-------|-------|-------|
| S_1 | S_0 | Y_3 | Y_2 | Y_1 | Y_0 |
| 0 | 0 | 0 | 0 | 0 | A |
| 0 | 1 | 0 | 0 | A | 0 |
| 1 | 0 | 0 | A | 0 | 0 |
| 1 | 1 | A | 0 | 0 | 0 |

The Logical expression of the term Y is as follows :

$$Y_0 = \bar{S}_1 \bar{S}_0 A$$

$$Y_1 = \bar{S}_1 S_0 A$$

$$Y_2 = S_1 \bar{S}_0 A$$

$$Y_3 = S_1 S_0 A$$


iii. Logic circuit Diagram :-

• Logic diagram components we will use are :

i). AND gates

ii). NOT gates

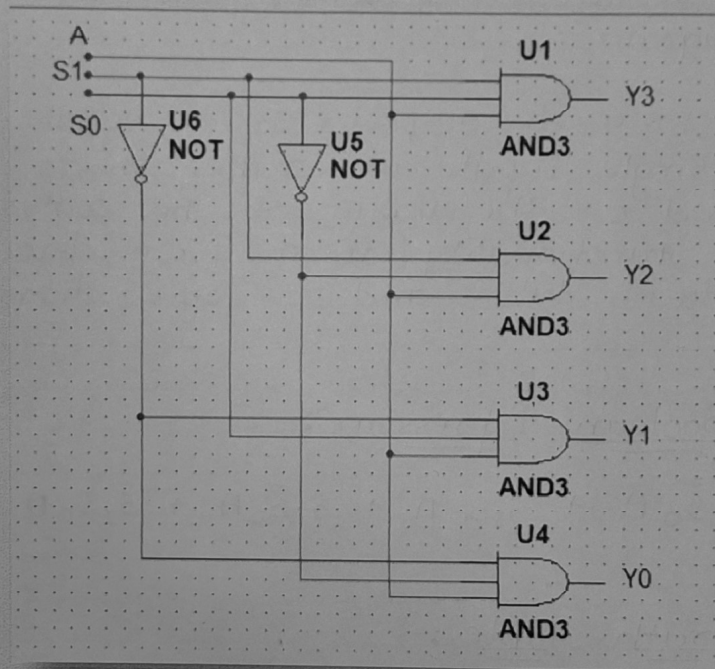Here, we will use four AND gates and two NOT gates.



Conclusion :-

In these experiment, we had done a verification of a 1-to-4 or 1×4 demultiplexer using truth tables and logic diagrams which provides a clear understanding of its functionality and operation.