

Sr No	Title	Date	Page No.	Marks	Sign
1.	To Verify the Behaviour of Logic Gates using Truth Table and Familiarization with Digital Integrated Circuits				
2.	To Verify Demorgan's theorem using Truth Table and Logic Diagram				
3.	To Verify Half adder and Full adder Truth Table and Logic Diagram				
4.	To Verify Half Subtractor & Full Subtractor using Truth Table and Logic Diagram				
5.	To Verify 4×1 Multiplexer using Truth Table and Logic Diagram				
6.	To Verify NAND & NOR as Universal Gate using Truth Table and Logic Diagram				
7.	To Verify 1×4 Demultiplexer using Truth Table and Logic Diagram				
8..	To Verify 3×8 Decoder using Truth Table and Logic Diagram				
9.	To Verify Gray to Binary Code Converter Decoder using Truth Table and Logic Diagram				
10.	To Verify 1 bit and 2 bit magnitude comparator using Truth Table and Logic Diagram				